

# Analog Electronics

**FOR EC/EE  
ESE & GATE**


**WORK BOOK  
PART 2**

Q1

**Objective:** Determine the currents and voltages in a half-wave rectifier circuit.

Consider the circuit shown in Figure . Assume  $V_B = 12 \text{ V}$ ,  $R = 100 \Omega$ , and  $V_y = 0.6 \text{ V}$ . Also assume  $v_S(t) = 24 \sin \omega t$ . Determine the peak diode current, maximum reverse-bias diode voltage, and the fraction of the cycle over which the diode is conducting.

**Aus 32.4%**

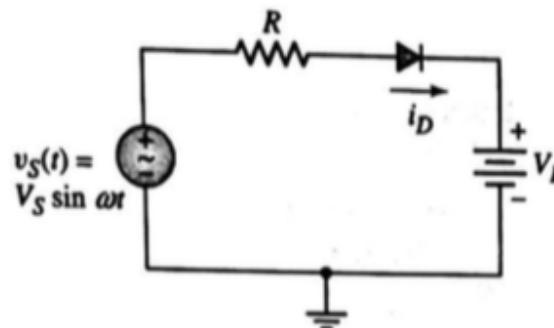

Q2

Repeat **about Q** if the peak sinusoidal voltage is  $V_S = 30 \text{ V}$  and the resistor is  $R = 200 \Omega$ . All other parameters are the same.

**Aus 36.2%**


Q3

Consider the bridge circuit shown in Figure with an input voltage  $v_S = V_M \sin \omega t$ . Assume a diode cut-in voltage of  $V_y = 0.7 \text{ V}$ . Determine the fraction (percent) of time that the diode  $D_1$  is conducting for peak sinusoidal voltages of (a)  $V_M = 12 \text{ V}$  and (b)  $V_M = 4 \text{ V}$ .

**Aus**

**(a) 46.3%**

**(b) 38.3%**

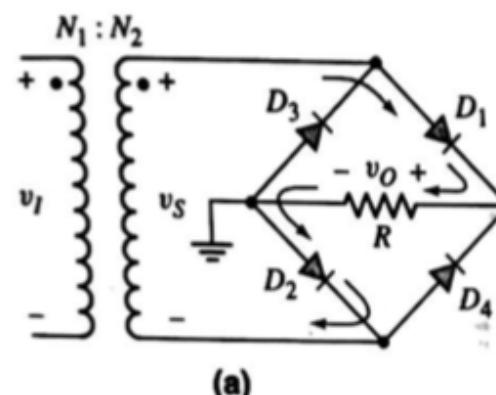

Q4

**Objective:** Determine the capacitance required to yield a particular ripple voltage.

Consider a full-wave rectifier circuit with a 60 Hz input signal and a peak output voltage of  $V_M = 10 \text{ V}$ .

Assume the output load resistance is  $R = 10 \text{ k}\Omega$  and the ripple voltage is to be limited to  $V_r = 0.2 \text{ V}$ .

**Aus 41.7uf**

Q5

Assume the input signal to a full-wave rectifier has a peak value of  $V_M = 24 \text{ V}$  and is at a frequency of 60 Hz. Assume the output load resistance is  $R = 1 \text{ k}\Omega$  and the ripple voltage is to be limited to  $V_r = 0.4 \text{ V}$ . Determine the capacitance required to yield this specification.

**Aus 500uf**

Q6



The circuit in Figure (a) is used to rectify a sinusoidal input signal with a peak voltage of 120 V and a frequency of 60 Hz. A filter capacitor is connected in parallel with  $R$ . If the output voltage cannot drop below 100 V, determine the required value of the capacitance  $C$ . The transformer has a turns ratio of  $N_1 : N_2 = 1 : 1$ , where  $N_2$  is the number of turns on each of the secondary windings. Assume the diode cut-in voltage is 0.7 V and the output resistance is  $2.5 \text{ k}\Omega$ .

$$\text{Ans } C = 20.6 \mu\text{F}$$

Q7

The secondary transformer voltage of the rectifier circuit shown in Figure (b) is  $v_s = 50 \sin[2\pi(60)t] \text{ V}$ . Each diode has a cut-in voltage of  $V_y = 0.7 \text{ V}$ , and the load resistance is  $R = 10 \text{ k}\Omega$ . Determine the value of the filter capacitor that must be connected in parallel with  $R$  such that the ripple voltage is no greater than  $V_r = 2 \text{ V}$ .


$$\text{Ans } 20.3 \mu\text{F}$$

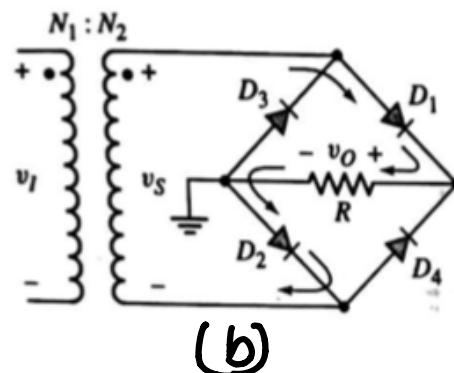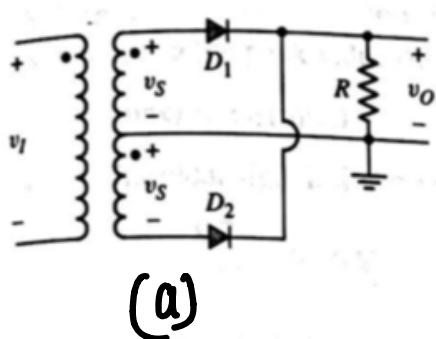

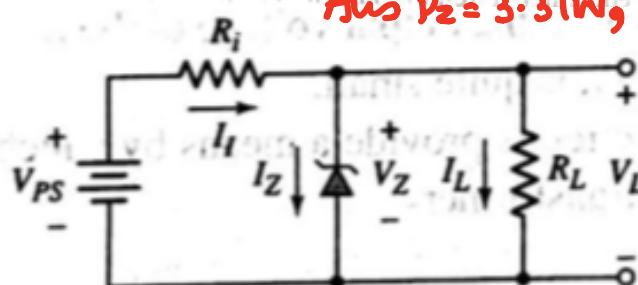Q8

The Zener diode regulator circuit shown in Figure 2.18 has an input voltage that varies between 10 and 14 V, and a load resistance that varies between  $R_L = 20$  and  $100 \Omega$ . Assume a 5.6 Zener diode is used, and assume  $I_Z(\min) = 0.1 I_Z(\max)$ . Find the value of  $R_i$  required and the minimum power rating of the diode.

$$\text{Ans } P_Z = 3.31 \text{ W}, R_i = 13 \Omega$$



Q9

**Objective:** Determine the source regulation and load regulation of a voltage regulator circuit.

Consider the circuit described in **above Q8** and assume a Zener resistance of  $r_z = 2 \Omega$ .

$$\text{Source Reg} = \frac{\Delta V_L}{\Delta V_{\text{source}}} \times 100\%$$

$$\text{Ans } 11.6\% - \text{Source Reg}$$


$$1.89 - \text{load Reg}$$

$$\text{load Reg} = \frac{V_{NL} - V_{FL}}{V_{PL}}$$

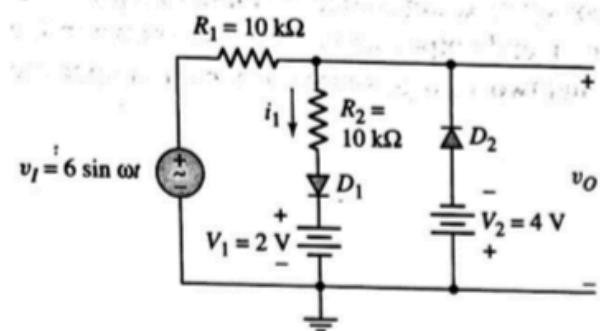
Q10

Objective: Find the output of the parallel-based clipper in Figure

For simplicity, assume that  $V_y = 0$  and  $r_f = 0$  for both diodes.




Aus

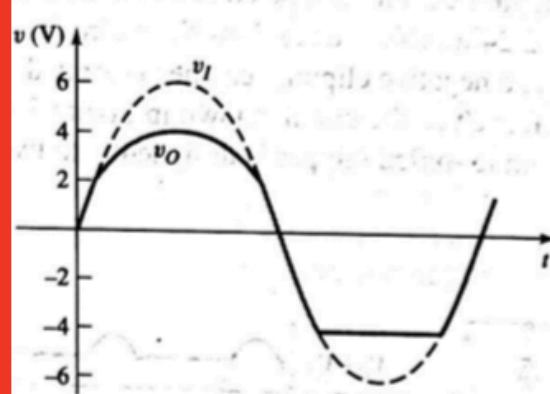

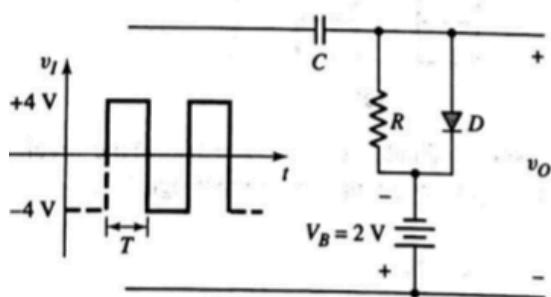Q11

Sketch the steady-state output voltage for the input signal given for the circuit in Figure. Assume  $V_y = r_f = 0$ .





Aus square b/w  
-2 to 10

Q12

Determine the steady-state output voltage  $v_O$  for the circuit in Figure shown in Figure (b). Assume the diode cut-in voltage is  $V_y = 0$ .

(a), if the input is as

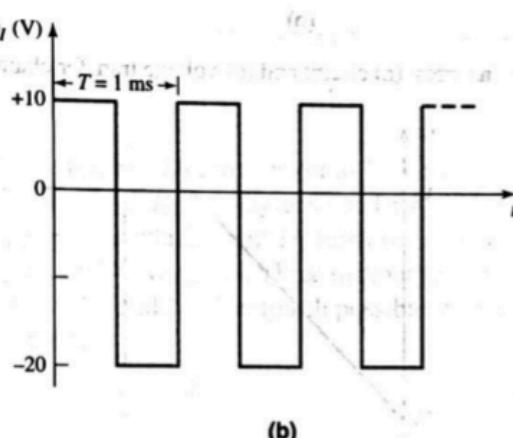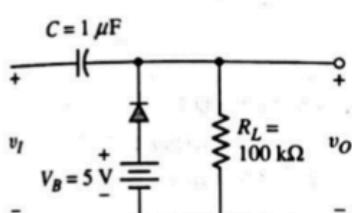


Aus square  
b/w +5 and  
-5
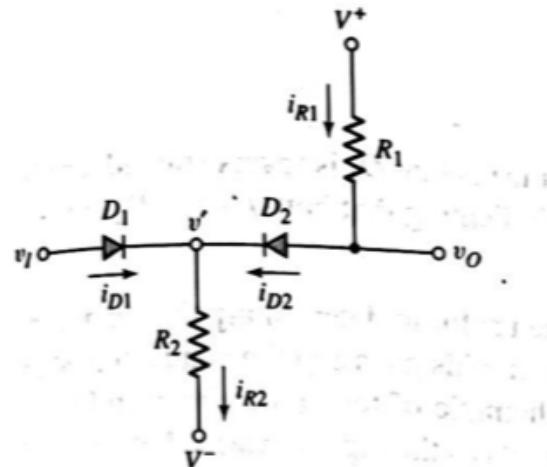
### Q13

**Objective:** Determine the output voltage and diode currents for the circuit shown in Figure for two values of input voltage.

Assume the circuit parameters are  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $V_y = 0.7 \text{ V}$ ,  $V^+ = +5 \text{ V}$ , and  $V^- = -5 \text{ V}$ . Determine  $v_O$ ,  $i_{D1}$ , and  $i_{D2}$  for  $v_I = 0$  and  $v_I = 4 \text{ V}$ .




$$\text{Ans } V_I = 0 \quad (D_1 = 0, i_{D2} = 0.62 \text{ mA}, v_O = 1.9 \text{ V})$$

$$V_I = 4 \quad i_{D1} = 0.63 \text{ mA} \quad i_{D2} = 0.2 \text{ mA} \quad v_O = V_I$$
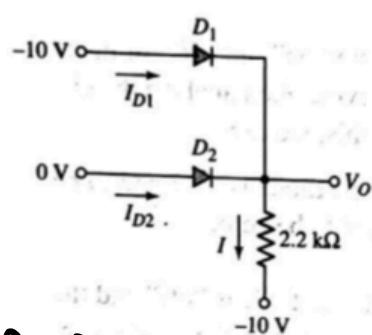
### Q14

Determine  $V_O$ ,  $i_{D1}$ ,  $i_{D2}$ , and  $I$  in the circuit shown in Figure . Assume  $V_y = 0.6 \text{ V}$  for each diode.




$$\text{Ans } V_O = -0.6 \text{ V}$$

$$i_{D1} = 0$$

$$i_{D2} = I = 4.27 \text{ mA}$$
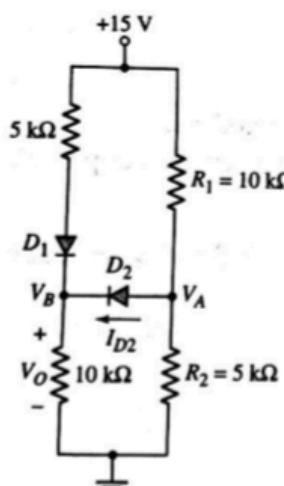
### Q15

**Objective:** Determine the current  $i_{D2}$  and the voltage  $V_O$  in the multidiode circuit shown in Figure . Assume  $V_y = 0.7 \text{ V}$  for each diode.




$$\text{Ans } i_{D2} = -7.86 \text{ mA}$$

Q16

Objective: Determine the current in each diode and the voltages  $V_A$  and  $V_B$  in the multidiode circuit shown in Figure. Let  $V_y = 0.7\text{ V}$  for each diode.

Aus

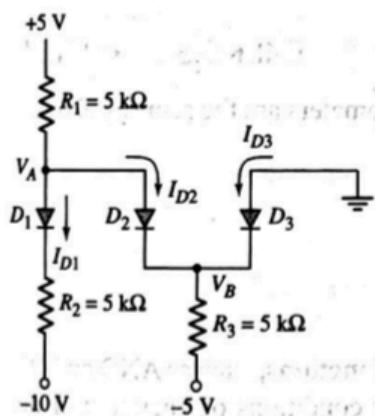


$$I_{D1} = 1.43 \quad I_{D2} = 0$$

$$I_{D3} = 0.86\text{mA}$$

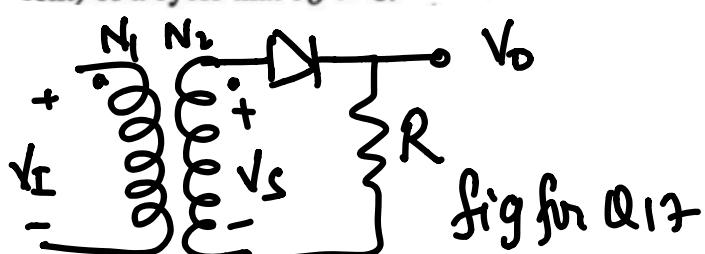Q17

Consider the half-wave rectifier circuit in Figure. The input voltage is  $v_I = 80 \sin[2\pi(60)t]\text{V}$  and the transformer turns ratio is  $N_1/N_2 = 6$ . If  $V_y = 0$  and  $r_f = 0$ , determine (a) the peak diode current, (b) the value of PIV, (c) the average value of the output voltage, and (d) the fraction (per cent) of a cycle that  $v_O > 0$ .



$$\text{Aus a) } i_{dm\max} = 13.3\text{A}$$

$$\text{b) PIV} = 13.3\text{ V}$$

$$\text{c) } V_{O(\text{avg})} = 4.24\text{V}$$

$$\text{d) } 50\%$$

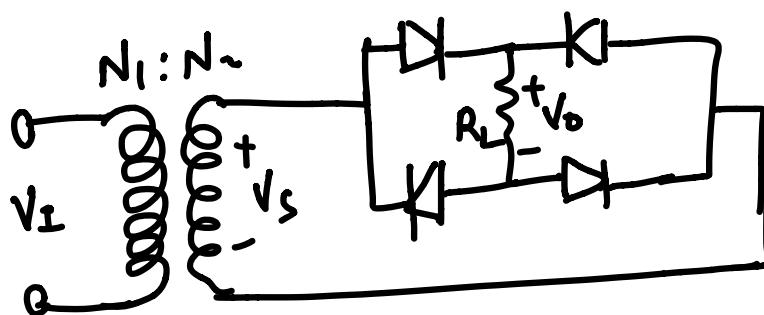


figure for Q18


Q18

The output resistance of the full-wave rectifier in Figure \_\_\_\_\_ in the text is  $R = 150 \Omega$ . A filter capacitor is connected in parallel with  $R$ . Assume  $V_y = 0.7$  V. The peak output voltage is to be 12 V and the ripple voltage is to be no more than 0.3 V. The input frequency is 60 Hz. (a) Determine the required rms value of  $v_s$ . (b) Determine the required filter capacitance value. (c) Determine the peak current through each diode.

*Ans (a) 9.48V (b) 2224F (c) 2.33A*

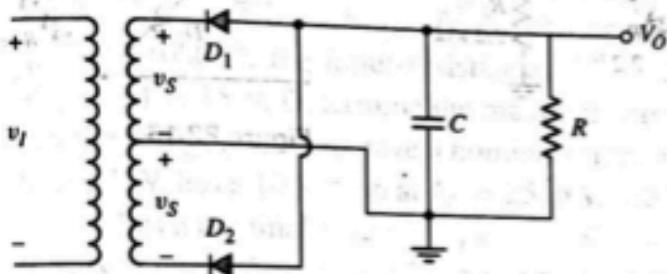Q19

The full-wave rectifier circuit shown in Figure \_\_\_\_\_ has an input signal whose frequency is 60 Hz. The rms value of  $v_s = 8.5$  V. Assume each diode cut-in voltage is  $V_y = 0.7$  V. (a) What is the maximum value of  $V_o$ ? (b) If  $R = 10 \Omega$ , determine the value of  $C$  such that the ripple voltage is no larger than 0.25 V. (c) What must be the PIV rating of each diode?




*Ans (a) 11.3V*

*(b) C = 0.03767F*

*(c) 233V*

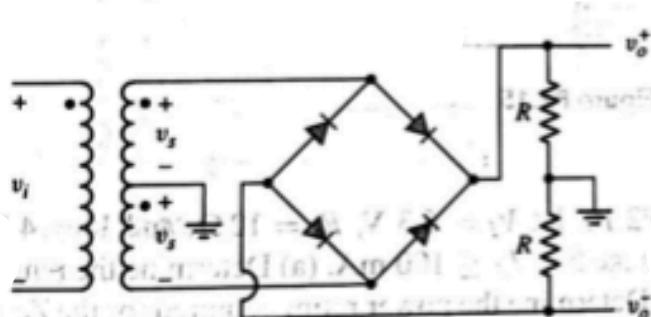Q20

The circuit in Figure \_\_\_\_\_ is a complementary output rectifier. If  $v_s = 26 \sin [2\pi(60)t]$  V, sketch the output waveforms  $v_o^+$  and  $v_o^-$  versus time, assuming  $V_y = 0.6$  V for each diode.




*Ans  $v_o^+ = |V_i|$*

*$v_o^- = -|V_i|$*

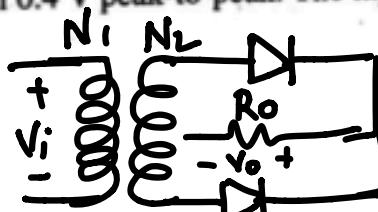Q21

The full-wave rectifier in Figure \_\_\_\_\_ is to deliver 0.1 A and 15 V (peak values) to a load. The ripple voltage is to be no larger than 0.4 V peak-to-peak. The input signal is 120 V (rms) at 60 Hz.





Assume diode cut-in voltages of 0.7 V. (a) Determine the required turns ratio. (b) the filter capacitance value, and (c) the diode PIV rating.

*Aus (a)  $N_1/N_2 = 10.8$*

*(b) 20f3uF (c) 30.7V*

Q22


Sketch  $v_o$  versus time for the circuit in Figure. The input is a sine wave given by  $v_i = 10 \sin \omega t$  V. Assume  $V_y = 0$ . (b) Determine the rms value of the output voltage.

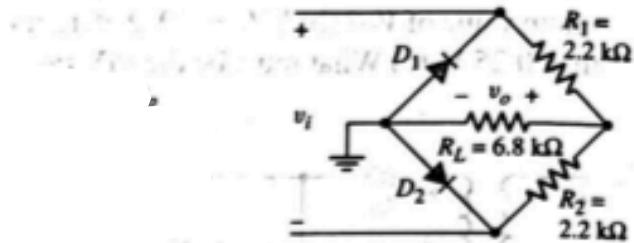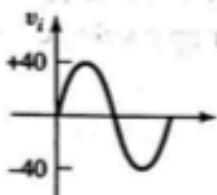

*Aus 3.04V.*

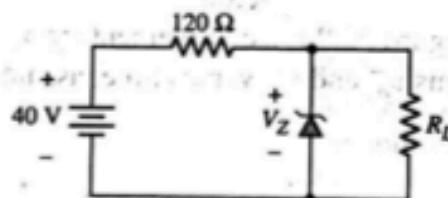Q23

Consider the Zener diode circuit shown in Figure P2.15. Assume  $V_Z = 12$  V and  $r_z = 0$ . (a) Calculate the Zener diode current and the power dissipated in the Zener diode for  $R_L = \infty$ . (b) What is the value of  $R_L$  such that the current in the Zener diode is one-tenth of the current supplied by the 40 V source?



*Aus  
(a) 0.233A,  
2.8W  
(b) R\_L = 57.1Ω*

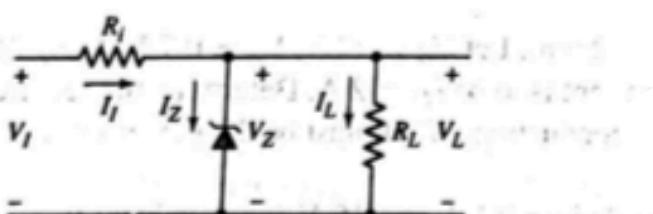


fig for Q24

- Q24** In the voltage regulator circuit in Figure P2.16,  $V_I = 20$  V,  $V_Z = 10$  V,  $R_i = 222 \Omega$ , and  $P_Z(\text{max}) = 400 \text{ mW}$ . (a) Determine  $I_L$ ,  $I_Z$ , and  $I_I$ , if  $R_L = 380 \Omega$ . (b) Determine the value of  $R_L$  that will establish  $P_Z(\text{max})$  in the diode.

Aus (a)  $I_L = 26.3 \text{ mA}$ ,  $I_Z = 18.3 \text{ mA}$ ,  $I_I = 45 \text{ mA}$   
 (b)  $R_L = 2 \text{ k}\Omega$

**Q25**

- A voltage regulator is to have a nominal output voltage of 10 V. The specified Zener diode has a rating of 1 W, has a 10 V drop at  $I_Z = 25 \text{ mA}$ , and has a Zener resistance of  $r_z = 5 \Omega$ . The input power supply has a nominal value of  $V_{PS} = 20 \text{ V}$  and can vary by  $\pm 25$  percent. The output load current is to vary between  $I_L = 0$  and  $20 \text{ mA}$ . (a) If the minimum Zener current is to be  $I_Z = 5 \text{ mA}$ , determine the required  $R_i$ . (b) Determine the maximum variation in output voltage. (c) Determine the percent regulation.

Aus  $200 \Omega$ ,  $3.5 \text{ V}$ ,  $3.5\%$ .

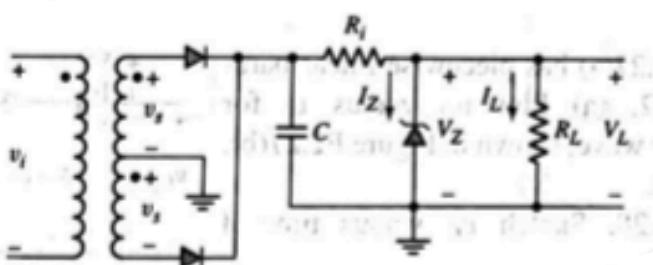


fig for Q26

**Q26**

- The secondary voltage in the circuit in Figure is  $v_s = 12 \sin \omega t$  V. The Zener diode has parameters  $V_Z = 8$  V at  $I_Z = 100 \text{ mA}$  and  $r_z = 0.5 \Omega$ . Let  $V_Y = 0$  and  $R_i = 3 \Omega$ . Determine the percent regulation for load currents between  $I_L = 0.2$  and  $1 \text{ A}$ . Find  $C$  such that the ripple voltage is no larger than 0.8 V.

Aus  $5\%$ , ( $= 0.035 \text{ F}$ )

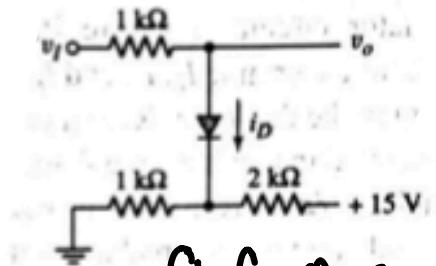


fig for Q27

Q27

For the circuit in Figure , plot  $v_o$  versus  $v_i$  for  $0 \leq v_i \leq 15$  V. Assume  $V_y = 0.7$  V. Indicate all breakpoints. (b) Plot  $i_D$  over the same range of input voltage.

$$\text{Ans}^{(a)} \quad v_o = v_i \text{ for } v_i \leq 5.7$$


$$v_o = \frac{v_i}{2.5} + 3.42 \quad 5.7 \leq v_i \leq 15$$

$$(b) \quad i_D = 0 \text{ for } v_i \leq 5.7$$

$$i_D = \frac{0.6v_i - 3.42}{1} \quad \text{for } 5.7 \leq v_i \leq 15$$

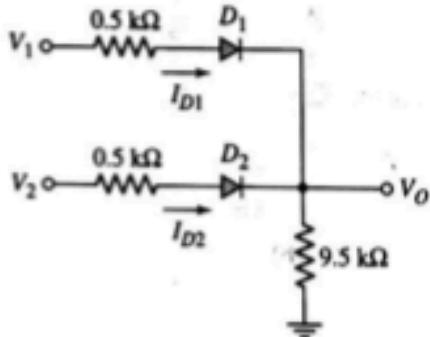Q28

The diodes in the circuit in Figure have piecewise linear parameters of  $V_y = 0.6$  V and  $r_f = 0$ . Determine the output voltage  $V_O$  and the diode currents  $I_{D1}$  and  $I_{D2}$  for the following input conditions: (a)  $V_1 = 10$  V,  $V_2 = 0$ ; (b)  $V_1 = 5$  V,  $V_2 = 0$ ; (c)  $V_1 = 10$  V,  $V_2 = 5$  V; and (d)  $V_1 = 10$  V,  $V_2 = 10$  V.



Aus

$$(a) I_{D1} = 0.94 \text{ mA}, I_{D2} = 0 \text{ mA} \\ V_O = 8.93 \text{ V}$$


$$(b) I_{D1} = 0.44 \text{ mA}, I_{D2} = 0 \text{ mA} \\ V_O = 4.18 \text{ V}$$

(c) Same as (a)

$$(d) I_{D1} = I_{D2} = 0.482 \text{ mA} \\ V_O = 9.16 \text{ V}$$

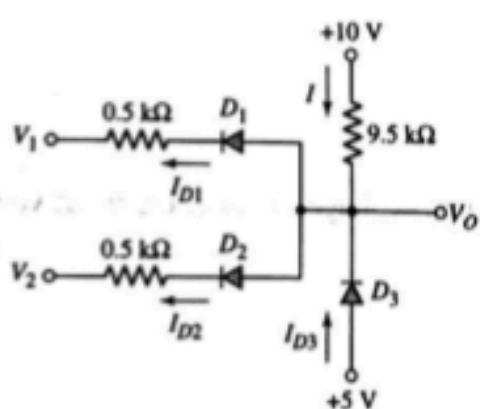Q29

The diodes in the circuit in Figure have the same piecewise linear parameters as described in Problem Q28. Determine the output voltage  $V_O$  and the currents  $I_{D1}$ ,  $I_{D2}$ ,  $I_{D3}$ , and  $I$  for the following input conditions: (a)  $V_1 = V_2 = 0$ ; (b)  $V_1 = V_2 = 5$  V; (c)  $V_1 = 5$  V,  $V_2 = 0$ ; and (d)  $V_1 = 5$  V,  $V_2 = 2$  V.




Aus

	$I_{D1}$	$I_{D2}$	$I_{D3}$
(a)	7.6 mA	7.6 mA	14.6 mA
(b)	0.2255	0.2255 mA	0
(c)	0	7.6 mA	7.01 mA
(d)	0	3.6 mA	3.01 mA

Q30

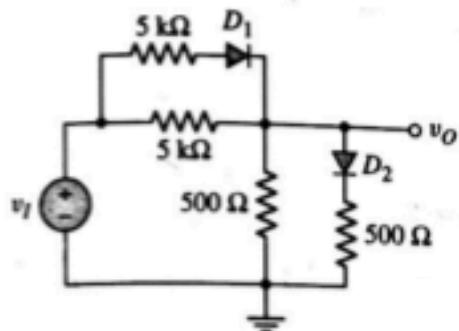(a) For the circuit in Figure  
 $0 \leq v_I \leq 10 \text{ V}$ .

each diode has  $V_y = 0.6 \text{ V}$ . Plot  $v_O$  versus  $v_I$  over the range



$$v_O = 0.0909 v_I \quad 0 \leq v_I \leq 0.66 \text{ V}$$


$$v_O = \frac{2v_I - 0.6}{12} \quad 0.66 \leq v_I \leq 3.9 \text{ V}$$

$$v_O = \frac{2v_I + 5.4}{22} \quad 3.9 \leq v_I \leq 10 \text{ V}$$

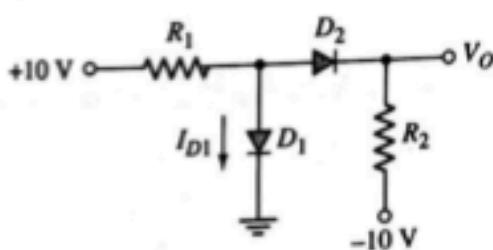Q31

Let  $V_y = 0.7 \text{ V}$  for each diode in the circuit in Figure  
(b) Repeat part (a) for  $R_1 = 10 \text{ k}\Omega$  and  $R_2 = 5 \text{ k}\Omega$ .

Find  $I_{D1}$  and  $V_O$  for  $R_1 = 5 \text{ k}\Omega$  and



Ans

(a)  $v_O = 0$   $I_{D1} = 0.86 \text{ mA}$


(b)  $I_{D1} = 0$ ,  $v_O = -3.57 \text{ mA}$

Q32

Assume each diode cut-in voltage is  $V_y = 0.7 \text{ V}$  for the circuit in Figure

$V_o$  for (a)  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 5 \text{ k}\Omega$  and (b)  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ .

Determine  $I_{D1}$  and

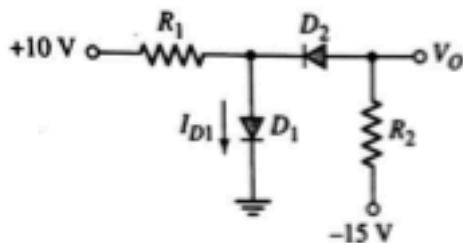

Aus

(a)  $I_{D1} = 0.93 \text{ mA}$   $V_o = -1.5 \text{ V}$


(b)  $I_{D1} = 1.86 \text{ mA}$   $V_o = -1.5 \text{ V}$

Q33

Let  $V_y = 0.6 \text{ V}$  for the diode in the circuit in Figure

$V_2 = 10 \text{ V}$ ; and (b)  $V_1 = 10 \text{ V}$ ,  $V_2 = 15 \text{ V}$ .

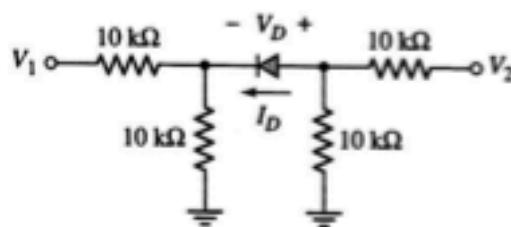Determine  $I_D$  and  $V_D$  if: (a)  $V_1 = 15 \text{ V}$ ,




Aus

(a)  $I_D = 0$ ,  $V_D = -2.5 \text{ V}$

(b)  $V_D = 0.6 \text{ V}$ ,  $I_D = 0.19 \text{ mA}$

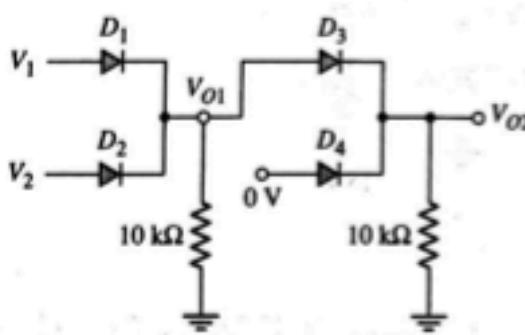Q34

Consider the circuit in Figure . The output of a diode OR logic gate is connected to the input of a second diode OR logic gate. Assume  $V_y = 0.6 \text{ V}$  for each diode. Determine the outputs  $V_{O1}$  and  $V_{O2}$  for: (a)  $V_1 = V_2 = 0$ ; (b)  $V_1 = 5 \text{ V}$ ,  $V_2 = 0$ ; and (c)  $V_1 = V_2 = 5 \text{ V}$ . What can be said about the relative values of  $V_{O1}$  and  $V_{O2}$  in their "high" state?



Aus

(a)  $V_{O1} = V_{O2} = 0$

(b)  $V_{O1} = 4.4 \text{ V}$ ,  $V_{O2} = 3.8 \text{ V}$

(c)  $V_{O1} = 4.4 \text{ V}$ ,  $V_{O2} = 3.8 \text{ V}$ .

